



**MAULANA ABUL KALAM AZAD UNIVERSITY OF
TECHNOLOGY, WEST BENGAL**

Paper Code : EE-301

ELECTRIC CIRCUIT THEORY

Time Allotted: 3 Hours

Full Marks: 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

Group – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for *any ten* of the following:

1×10=10


(i) When compared to a first-order low pass filter, a second-order low pass filter has

- | | |
|------------------------------------|------------------------------|
| (a) low voltage gain | (b) higher voltage gain |
| (c) faster drop in filter response | (d) higher cut-off frequency |

(ii) $F(s) = (1 - e^{-st})/s$ is the Laplace transform of

- | | |
|------------------------------|-------------------------------|
| (a) a pulse of width T | (b) a square wave of period T |
| (c) a unit step delayed by T | (d) a ramp delayed by T |

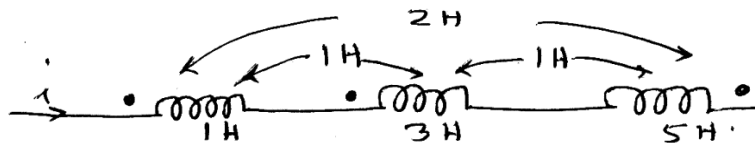(iii) The total inductance of the three series connected coupled coils is




- | | |
|---------|---------|
| (a) 6 H | (b) 5 H |
| (c) 7 H | (d) 8 H |

(iv) The output Y and input X of a system are related by the equation $Y = mX + c$, where m, c are constant. The system is

- (a) linear (b) non-linear
(c) bilateral (d) unilateral

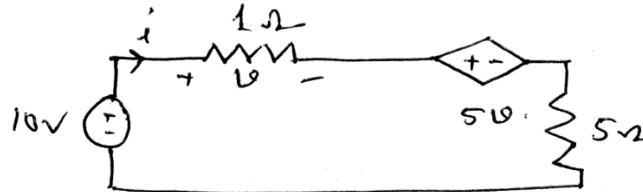(v) The current ' i ' in the circuit shown is given by



- (a) 10 A (b) 5 A
(c) 2 A (d) 20 A



(vi) When a unit impulse voltage is applied to an inductor of 1H, the energy supplied by the source is

- (a) $\propto J$ (b) 1 J
(c) $\frac{1}{2} J$ (d) 0 J

(vii) An initially relaxed RC series circuit with $R = 2M\Omega$ and $C = 1\mu F$ is switched to a 10V step input. The voltage across the capacitor after 2 seconds will be

- (a) 0V (b) 3.68V
(c) 6.32V (d) 10V

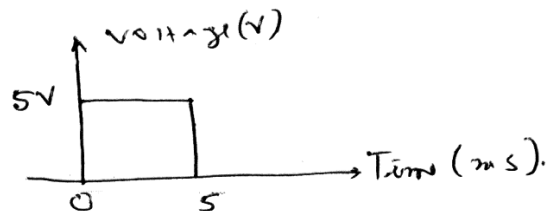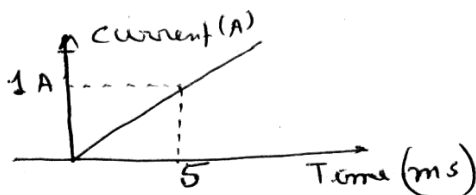(viii) The current and voltage profile of a circuit element vs time is shown in the figure. The element is



- (a) inductor (b) capacitor
(c) resistor (d) transistor


(ix) The V - S characteristic of a resistor is $i = 2v^2$. The resistor is

- (a) linear, passive, bilateral (b) nonlinear, active, bilateral
(c) nonlinear, passive, bilateral (d) nonlinear, active, unilateral

(x) For a connected planar graph of v vertices and e edges, the number of meshes is

- (a) $e - v + 1$ (b) $e + v + 1$
(c) $e + v - 1$ (d) $e - v - 1$

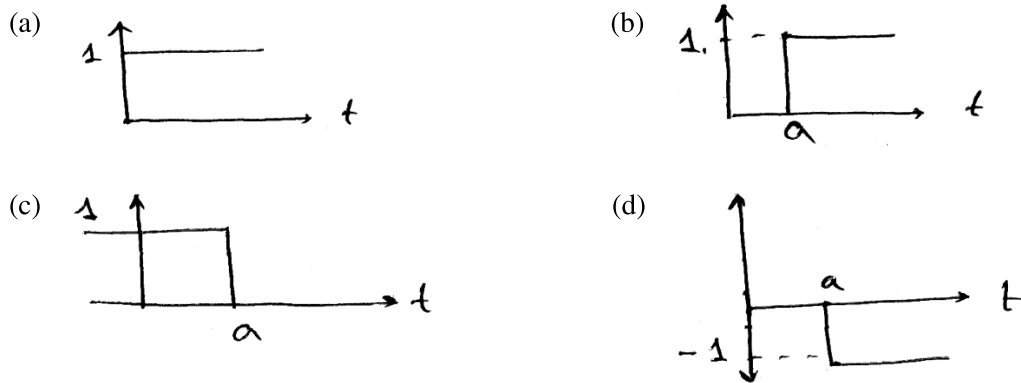(xi) The graphical representation of $u(a - t)$ is given by



(xii) At steady state condition, the inductor and capacitor will behave as respectively

- (a) short circuit, open circuit (b) open circuit, short circuit
(c) both open circuit (d) both short circuit


Group – B

(Short Answer Type Questions)


Answer any three of the following.

5×3=15

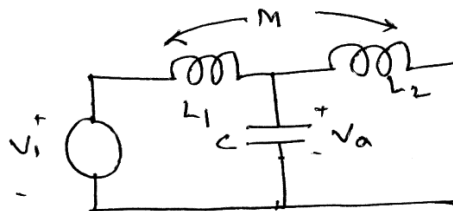
2. In the circuit shown below, $V_1(t) = 2\cos t$, $c = 1F$, $L_1 = L_2 = 1H$ and $M = \frac{1}{4}N$. Find the voltage $V_a(t)$.



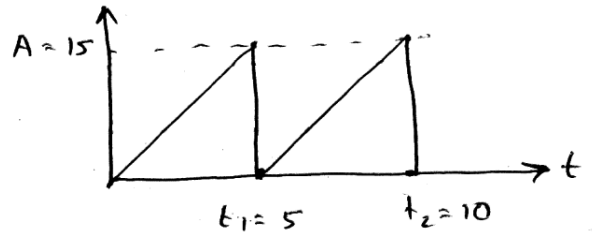3. Find the Laplace transform of the following waveform.




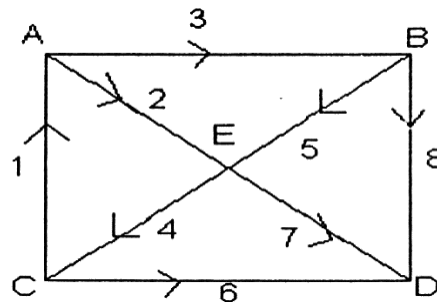4. ~~Consider the circuit shown in the figure.~~ Draw the corresponding graph. Find the complete incident matrix and the reduce incident matrix. Find the possible no. of trees.



5. Draw the circuit of a second order low pass filter and calculate its cut off frequency for $R = 34 \text{ k}\Omega$ and $c = 0.0047 \mu\text{F}$.

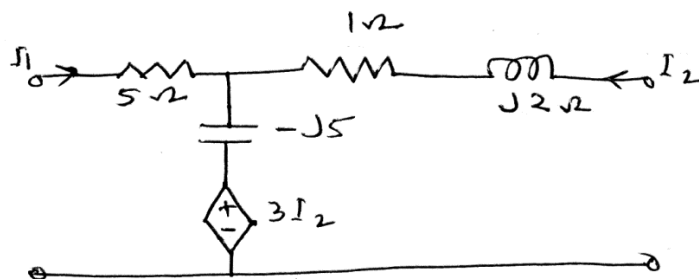6. Find the Z-parameters of the circuit given below.




Group – C

(Long Answer Type Questions)


Answer any three of the following.

15×3=45

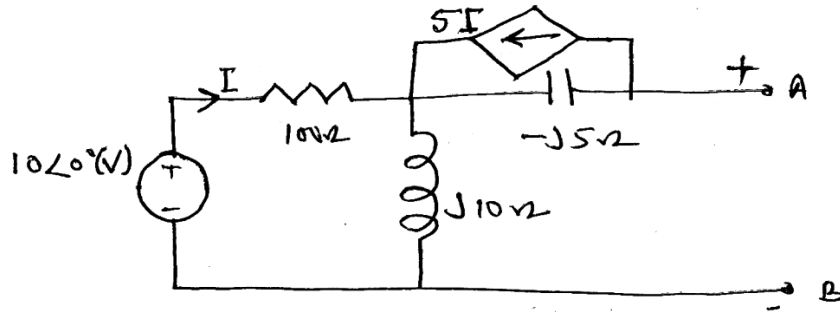
7. (a) Compute Thevenin equivalent of the network shown:



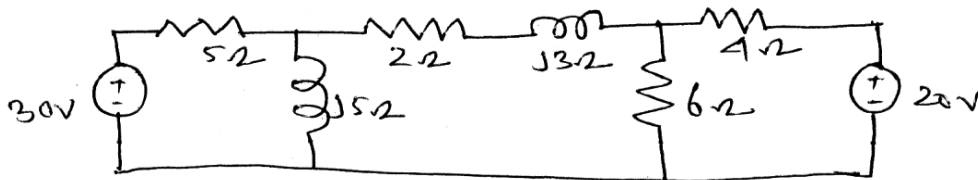- (b) Using superposition theorem, calculate the current through the $(2 + j3)$ ohm impedance of the circuit shown:




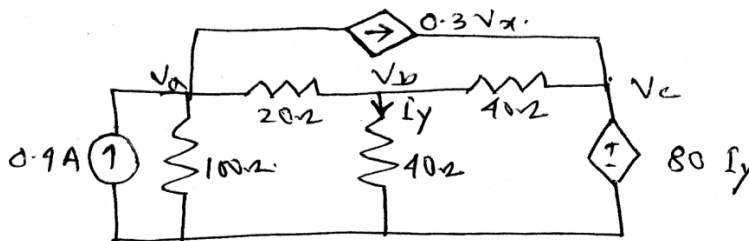- (c) Use Nodal analysis method to find the voltages V_a , V_b , and V_x in the circuit shown.




5+5+5=15

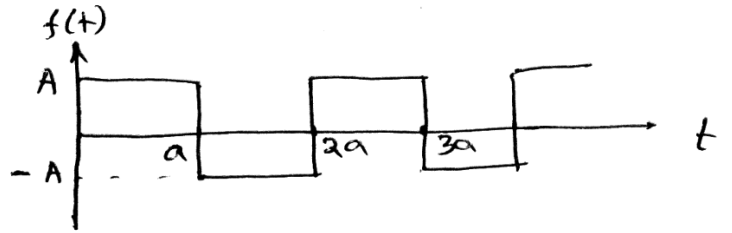8. (a) Find the Laplace transform of the square wave shown below:




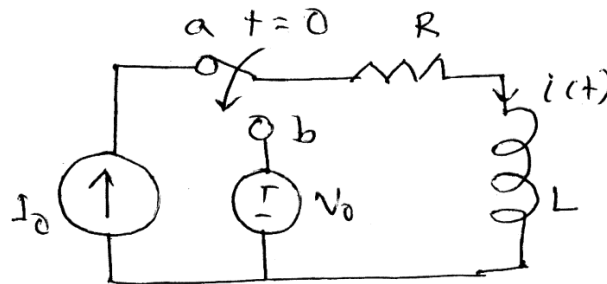- (b) In the circuit shown below, the switch moves from position 'a' to position 'b' at $t = 0$. Find $i(t)$ for time $t > 0$.




- (c) Mention differences between the Laplace transform and the Fourier transform. What are the application of these transforms. 5+5+5=15

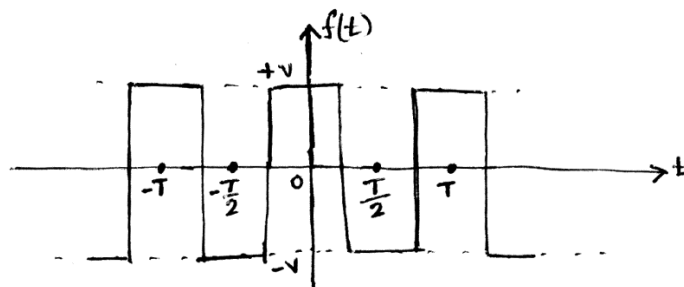9. (a) Write down the conditions which a periodic function must satisfy to have its Fourier series expansion.
- (b) Write down the trigonometric form of the Fourier series for a function $f(t)$ and evaluate various Fourier Coefficients.
- (c) Determine the Fourier series for the square waveform shown in the figure and plot the magnitude and phase spectra. 2+5+8=15



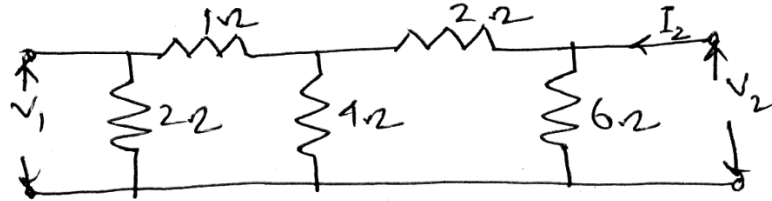10. (a) Find the Y parameter of the network shown:




- (b) Deduce the conditions for symmetry for the hybrid parameters of 2 port network.

- (c) What are ABCD parameters? Prove that $AD - BC = 1$.

5+5+5=15

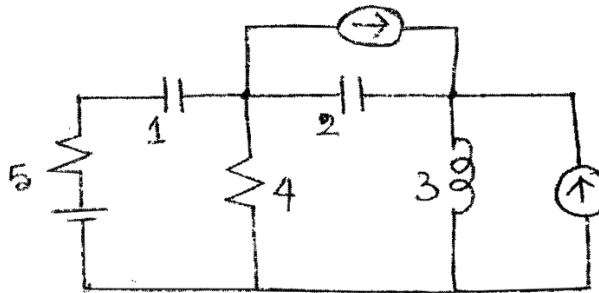11. (a) Define incidence matrix. For the network shown in figure, construct the complete incidence matrix.



- (b) For the same network shown in figure, determine all the tree and co-tree. Then considering the tree formed by branches 1, 2, 5 construct cut-set matrix and tie-set matrix.

(1+4)+10=15